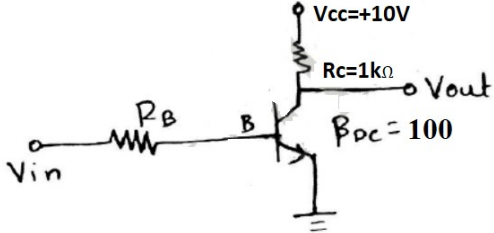
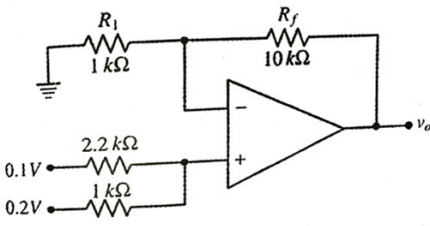
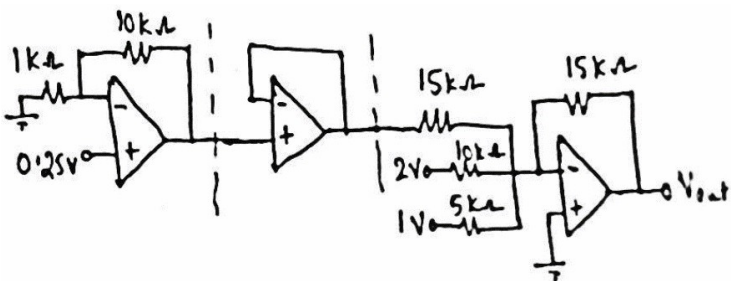



CONTINUOUS INTERNAL EVALUATION- 2

Dept: FY	Sem / Div: II A/B/C	Sub: Basic Electronics	S Code:18ELN24
Date:1/09/2021	Time: 9:30-11:00 am	Max Marks: 50	Elective: N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	COs
PART A				
1 a	Explain voltage series feedback circuit and derive an equation for voltage gain A_v with feedback	8	L2	CO1
b	Explain op-amp as Differentiator with a neat circuit diagram.	8	L2	CO3
c	The transistor in CE configuration with $R_c=1k\Omega$, $\beta_{dc}=100$. Determine (i) V_{ce} at $V_{in}=0v$ (ii) $R_{b(max)}$ when $V_{in}=8V$. $V_{ce(sat)}$ can be neglected.	4	L3	CO1
				
d	Explain different input modes of an op-amp.	5	L2	CO3
OR				
2 a	What is feedback amplifier? What are the properties and advantages of negative feedback amplifier.	8	L2	CO1
b	Explain the following terms with respect to op-amp. (i)Slew rate (ii)CMRR (iii)Input impedance (iv)Input bias current.	8	L2	CO3
c	Explain how BJT can be used as a switch.	4	L2	CO1
d	Calculate the output voltage of op-amp circuit shown.	5	L3	CO3
				
PART B				
3 a	Calculate the output Voltage for the circuit shown below	8	L3	CO3
				

CONTINUOUS INTERNAL EVALUATION- 2

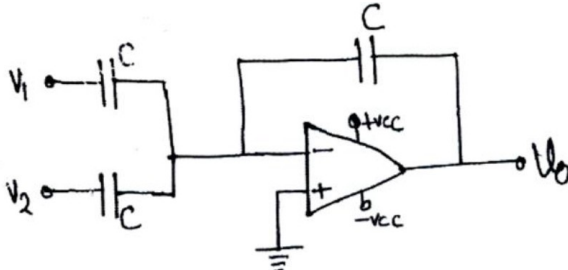b	Design an op-amp circuit to get output voltage of $V_0 = -(0.2V_1 + 0.45V_2 + 20V_3)$. Select $R_f = 30k\Omega$	8	L3	CO3
c	Explain a simple application of a transistor switch.	4	L2	CO1
d	Derive the relationship between gain and bandwidth of feedback amplifier.	5	L2	CO1
OR				
4 a	Explain the operation of op-amp as an inverting amplifier with a neat diagram and waveform.	8	L2	CO3
b	For an op-amp circuit shown find output voltage V_0	8	L3	CO3
				
c	In a transistor amplifier circuit determine the voltage gain and ac output voltage if $V_b = 200mV$, $R_c = 2k\Omega$ and $r_e = 45\Omega$.	4	L3	CO1
d	Derive an expression to show gain Stability increases with Feedback.	5	L2	CO1